Assignment

Course Code: CSE224
CourseTitle : DLD Lab

Submitted To

Name: Ms. Zahura Zaman

Department of: CSE

Daffodil International University

Submitted By:

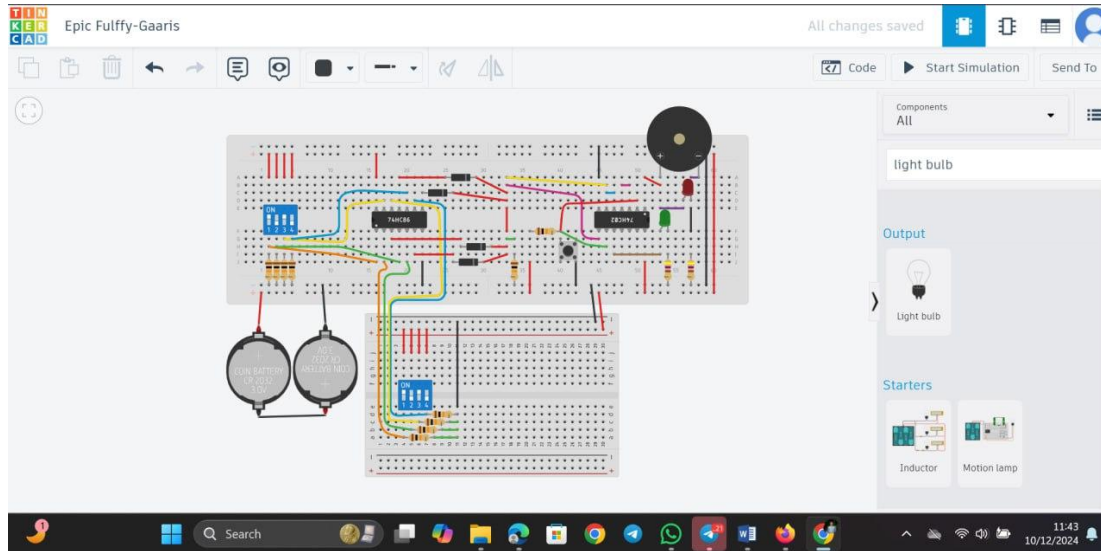Name: MD. Abdus Salam

ID: 0242310005101066

Section: 64-H

Department Of CSE

DaffodilInternationalUniversity
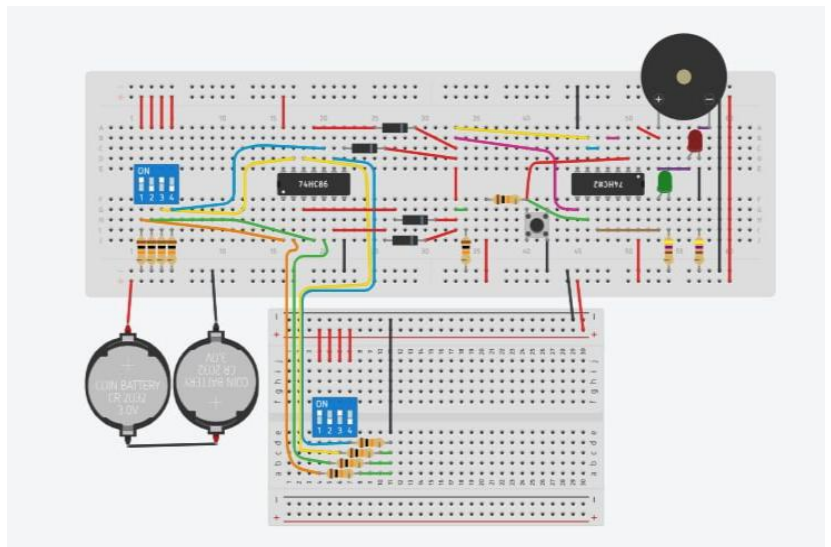
Date: 10.12..2024

4-Bit Password Security System

Tin Car Cad Image:

Tin Car Cad Link: [Click Heare](#)

Input Equipments:
- Quad XOR gate
- Quad NOR gate
- 2- DIP switch
- 10- 10k Resistor
- 2- 470 Resistor
- 4- 1N914 Didoes
- Pushbutton
- 2- led light (green and red)
- Buzzer
- 6V Battery
- Wires

Output Resut: It's Work Successfully.